

AC Voltage Controller



If a thyristor switch is connected between ac supply and load, the power flow can be controlled by varying the rms value of ac voltage applied to the load; this type of power circuit is known as an ac voltage source controller.

For power transfer, two types of controllers are used:

1. On-off controller: Thyristor switches connect the load to the ac source for a few cycles of input voltage and then disconnect it for another few cycles.
2. Phase controller: Thyristor switches connect to the load to the ac source for a portion of each cycle of input voltage. Types:

- i) single phase unidirectional controller
 - ii) single phase bidirectional controller
- } 1 ϕ
- iii) 3- ϕ unidirectional controller
 - iv) 3- ϕ bidirectional controller
- } 3- ϕ

On-off controller:

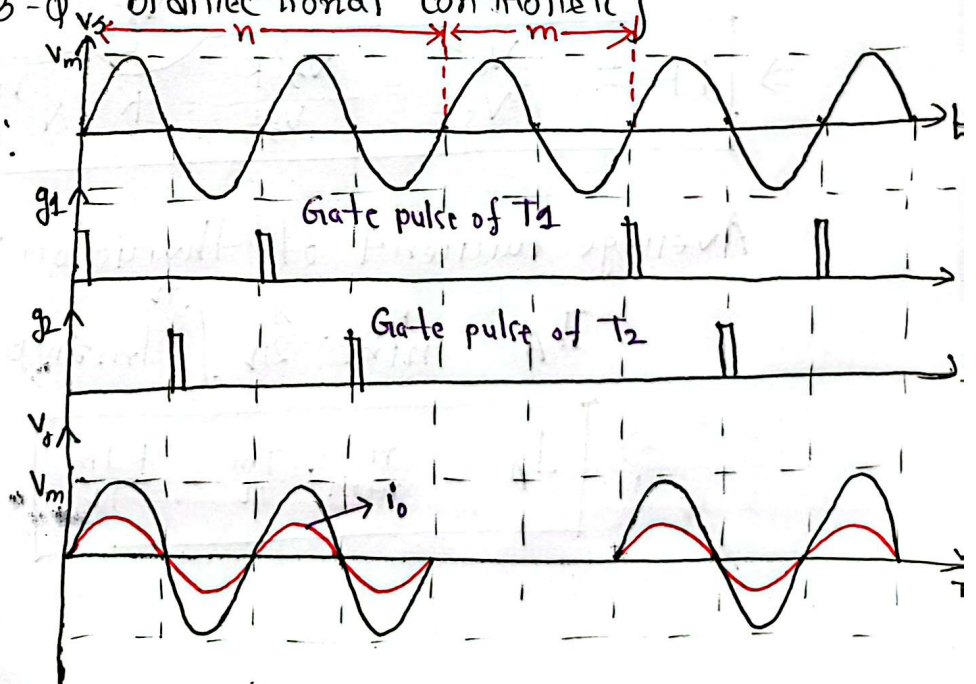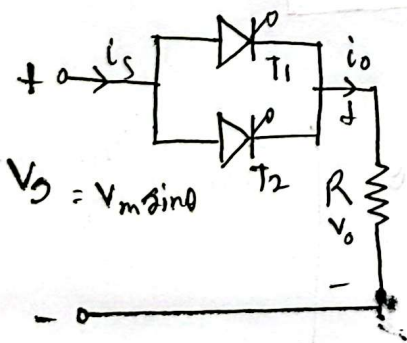

RMS output voltage:

$$\begin{aligned}
 V_o &= \sqrt{\frac{1}{T} \int_0^T V_s^2 d\theta} \\
 &= \left[\frac{n}{n+m} \cdot \frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \theta d\theta \right]^{1/2} \\
 &= \left[\frac{n}{n+m} \cdot \frac{V_m^2}{4\pi} \int_0^{2\pi} (1 - \cos 2\theta) d\theta \right]^{1/2} \\
 &= \left[\frac{n}{n+m} \cdot \frac{V_m^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{2\pi} \right]^{1/2} \\
 &= \left[\frac{n}{n+m} \cdot \frac{V_m^2}{4\pi} (2\pi - 0) \right]^{1/2} \\
 &= \left[\frac{n}{n+m} \cdot \frac{V_m^2}{4\pi} \cdot 2\pi \right]^{1/2} \\
 &= \sqrt{\frac{n}{n+m}} \cdot \frac{V_m}{\sqrt{2}}
 \end{aligned}$$

$$V_o = \sqrt{K} \cdot V_s$$

[K = duty cycle] $K = \frac{n}{n+m}$

$$PF = \frac{P_o}{V_A} = \frac{\frac{V_o^2}{R}}{V_s I_o} = \frac{\frac{V_o^2}{R}}{\frac{V_s^2}{R}}$$

$$\Rightarrow PF = \frac{V_o^2}{V_s^2} = \frac{V_s^2 K}{V_s^2} = K = \sqrt{\frac{n}{n+m}}$$

Average current of thyristor:

$$I_A = \frac{n}{n+m} \cdot \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \theta d\theta$$

$$I_m = \frac{V_m}{R} = \frac{\sqrt{2} V_s}{R}$$

$$\Rightarrow I_A = \frac{n}{n+m} \cdot \frac{I_m}{\pi} = \frac{K I_m}{\pi}$$

RMS current of thyristor:

$$I_R = \left[\frac{n}{n+m} \cdot \frac{1}{2\pi} \int_0^\pi I_m^2 \sin^2 \theta d\theta \right]^{1/2}$$

$$\Rightarrow \boxed{I_R = \frac{I_m \sqrt{K}}{2} = \frac{\sqrt{K}}{2} \cdot \frac{V_m}{R} = \sqrt{\frac{K}{2}} \cdot \frac{V_s}{R}}$$

Example 11.1: A ac voltage controller has a resistive load of $R = 10 \Omega$ and the rms input voltage is $V_s = 120V$, $60Hz$. The thyristor switch is on for $n = 25$ cycles and is off for $m = 75$ cycles. Determine the (a) rms output voltage V_o ; (b) input power factor, PF; and (c) average and rms current of thyristors.

Solⁿ: given that, $R = 10 \Omega$, $n = 25$ & $m = 75$, $V_s = 120V$

(a)

rms output voltage,

$$\begin{aligned} V_o &= V_s \cdot \sqrt{K} = V_s \sqrt{\frac{n}{n+m}} \\ &= 120 \cdot \sqrt{\frac{25}{25+75}} \\ &= 60V \end{aligned}$$

$$\begin{aligned} (b) \text{ PF} &= \frac{P_o}{P_A} = \frac{\frac{V_o^2}{R}}{V_s I_o} = \frac{\frac{V_o^2}{R}}{\frac{V_s^2}{R}} \quad [I_o = \frac{V_s}{R}] \\ &= \frac{V_o^2}{V_s^2} = \sqrt{K} = \frac{n}{n+m} = \sqrt{\frac{25}{100}} = \sqrt{0.25} = 0.5 \end{aligned}$$

$$(c) \quad I_m = \frac{V_m}{R} = \frac{\sqrt{2} V_s}{R} = \frac{\sqrt{2} \cdot 120}{10} = 12\sqrt{2}$$

$$\therefore \text{Average current } I_A = \frac{K I_m}{\pi} = \frac{0.25 \times 12\sqrt{2}}{\pi} = 1.35A$$

$$\therefore \text{rms current } I_R = \frac{I_m \sqrt{K}}{2} = \sqrt{\frac{K}{2}} \cdot \frac{V_s}{R} = \sqrt{\frac{0.25}{2}} \cdot \frac{120}{10} = 4.24A$$